

SI PREFIXES & UNITS

T / G / M / k	$10^{12} / 10^9 / 10^6 / 10^3$
m / μ / n / p	$10^{-3} / 10^{-6} / 10^{-9} / 10^{-12}$
A	C/s · V = J/C
W	J/s = V·A
S (siemens)	Ω^{-1} , conductance $G = 1/R$
kW·h	3.6×10^6 J

CHARGE · CURRENT · VOLTAGE

Current	$i(t) = \frac{dq}{dt}$
Charge	$q(t_1) = \int_{t_0}^{t_1} i dt + q(t_0)$
Constant i	$q = i \Delta t$
Double subscript	$v_{ab} = v_a - v_b$, $v_{ba} = -v_{ab}$
Reference	Polarity/direction is a <i>choice</i> . Negative answer $\Rightarrow$ true direction is opposite. Never re-draw, just report the sign.

POWER & PASSIVE SIGN CONVENTION

Power	$p = v i$ (W)
Energy	$w = \int_{t_0}^{t_1} p dt$ (J)
PSC	Current enters + terminal $\Rightarrow p = vi$ is power absorbed
Active config	Current exits + terminal $\Rightarrow p = -vi$; element supplies
Balance	$\sum p = 0$ over the whole circuit (supplied = absorbed) — always use as a check

OHM'S LAW & RESISTORS

Ohm	$v = iR$, $i = Gv$, $G = 1/R$
Dissipation	$p = vi = i^2 R = \frac{v^2}{R} \geq 0$ always
Geometry	$R = \frac{\rho L}{A}$, $\rho_{\text{copper}} = 1.72 \times 10^{-8} \Omega\text{m}$
Ideal wire	$R = 0 \Rightarrow$ zero drop; both ends are the same node
Open circuit	$i = 0$ (any v) · Short: $v = 0$ (any i)

KCL & KVL

KCL	$\sum i_{\text{in}} = \sum i_{\text{out}}$ at any node (charge conservation)
KVL	$\sum v = 0$ around any closed loop (energy conservation)
KVL rule	Traverse the loop; use the first polarity sign encountered ($+$ $\Rightarrow$ add, $-$ $\Rightarrow$ subtract)
Series	same current through every element
Parallel	same voltage across every element

SERIES / PARALLEL – ALL ELEMENTS

R series	$R_{eq} = \sum R_k$
R parallel	$\frac{1}{R_{eq}} = \sum \frac{1}{R_k}$; two: $\frac{R_1 R_2}{R_1 + R_2}$
L series	$L_{eq} = \sum L_k$; parallel $\frac{1}{L_{eq}} = \sum \frac{1}{L_k}$ (like R)
C series	$\frac{1}{C_{eq}} = \sum \frac{1}{C_k}$; parallel $C_{eq} = \sum C_k$ (opposite of R)
Z	series $Z_{eq} = \sum Z_k$; parallel $\frac{1}{Z_{eq}} = \sum \frac{1}{Z_k}$

DIVIDERS

Voltage divider	$V_n = \frac{R_n}{R_1 + \dots + R_N} V_{\text{total}}$ (series only)
Current divider	$i_1 = \frac{R_2}{R_1 + R_2} i_{\text{total}}$ (2 branches, parallel only)
General CD	$i_k = \frac{G_k}{\sum G} i_{\text{total}} = \frac{R_{eq}}{R_k} i_{\text{total}}$
Watch	VD: bigger R gets more v . CD: bigger R gets less i — the opposite resistor is on top.
AC form	Same formulas with Z in place of R .

NODE-VOLTAGE ANALYSIS

1	Pick reference (ground) — usually the $-$ terminal of the largest source / most-connected node.
2	Label $v_1, v_2, \dots$ at remaining nodes.
3	LEAVING — the course convention, keep it every time.
Branch term	$\frac{v_{\text{this}} - v_{\text{other}}}{R}$ (this node's v first)
To ground	$\frac{v_{\text{this}}}{R}$
Source at node	If v_s ties a node to ground: $v_1 = v_s$, write no KCL there.

SUPERNODES & DEPENDENT SOURCES

When	A voltage source sits between two <i>non-reference</i> nodes (its current is unknown).
Do	Draw a bubble around both nodes + the source; write one KCL for everything leaving the bubble .
Plus constraint	KVL across the source: $v_{(+ \text{ node})} - v_{(- \text{ node})} = V_s$
Dependent src	Treat as an ordinary source, then add the control equation expressing v_x or i_x in node voltages.
Never	Never deactivate a dependent source (superposition, R_{Th} — see those cards).

MESH-CURRENT ANALYSIS

1	Assign a mesh current to every window pane, all clockwise (course convention).
2	KVL around each mesh in the direction of its own current.
Own resistor	drop = $i_k R$
Shared resistor	drop = $(i_k - i_{\text{adj}})R$ — own current first
Current src in one mesh	$i_k = \pm I_s$ directly; skip that KVL.
Src between meshes	Supermesh : KVL around the outside of both, plus $i_k - i_j = I_s$.

THÉVENIN & NORTON

Thévenin	V_{Th} in series with R_{Th}
Norton	I_N in parallel with R_N
V_{Th}	$= v_{oc}$ with the load removed
I_N	$= i_{sc}$ with the terminals shorted
R_{Th}	$= R_N = \frac{v_{oc}}{i_{sc}}$
Source-kill R_{Th}	Only if no dependent sources : V -src $\rightarrow$ short, I -src $\rightarrow$ open, then reduce series/parallel.

SUPERPOSITION

Procedure	Leave one independent source on, deactivate the rest, solve; repeat; add all contributions <i>with sign</i> .
Deactivate	voltage source $\rightarrow$ short (0 V) · current source $\rightarrow$ open (0 A)
Dependent	ALWAYS left active in every sub-circuit.
NOT for power	$p \propto i^2$ is nonlinear — sum i first, <i>then</i> compute p .

WHEATSTONE BRIDGE

Layout	R_1, R_2 one leg; R_3, R_4 other leg; meter across the two midpoints.
Balanced	$\frac{R_1}{R_2} = \frac{R_3}{R_4} \Leftrightarrow R_1 R_4 = R_2 R_3$
At balance	$v_{\text{bridge}} = 0$, no current through the meter branch — it can be removed or shorted freely.
Unknown	$R_x = R_{\text{known}} \frac{R_2}{R_1}$

CAPACITORS

i–v	$i = C \frac{dv}{dt}$
v from i	$v(t) = \frac{1}{C} \int_0^t i d\tau + v(0)$
Energy	$w = \frac{1}{2} C v^2$ (stored, never dissipated)
Continuity	v_C cannot jump : $v_C(0^+) = v_C(0^-)$ (a jump needs infinite i); i_C can jump freely.
DC steady state	open circuit ($dv/dt = 0 \Rightarrow i = 0$)

INDUCTORS

v–i	$v = L \frac{di}{dt}$ (H)
i from v	$i(t) = \frac{1}{L} \int_0^t v d\tau + i(0)$
Energy	$w = \frac{1}{2} L i^2$
Continuity	i_L cannot jump : $i_L(0^+) = i_L(0^-)$ (a jump needs infinite v)
DC steady state	short circuit ($di/dt = 0 \Rightarrow v = 0$)

FIRST-ORDER TRANSIENTS

Universal	$x(t) = x(\infty) + [x(0^+) - x(\infty)]e^{-t/\tau}$
τ	RC: $\tau = R_{Th}C$ · RL: $\tau = L/R_{Th}$
R_{Th}	resistance seen by the C or L with sources deactivated, <i>after</i> the switch moves
Charging/discharge	Charging: $v_C = V_s(1 - e^{-t/\tau})$. Discharging: $v_C = V_0 e^{-t/\tau}$. Charging current: $i = \frac{V_s}{R} e^{-t/\tau}$.

TRANSIENT PROCEDURE & T TABLE

1	$t < 0$: old circuit at DC steady state (C open, L short) $\Rightarrow$ find $v_C(0^-) / i_L(0^-)$.
2	Continuity: $v_C(0^+) = v_C(0^-)$, $i_L(0^+) = i_L(0^-)$.
3	$t \rightarrow \infty$: new circuit at DC steady state $\Rightarrow x(\infty)$. τ from the new circuit's R_{Th} ; substitute into the
4	universal formula. Other quantities: get from v_C/i_L via Ohm/KVL, not another exponential.
Solve for t	$t = -\tau \ln \frac{x(t) - x(\infty)}{x(0^+) - x(\infty)}$

AC SINUSOIDS & RMS

Course form	$v(t) = V_m \sin(\omega t + \theta)$
ω	$= 2\pi f = \frac{2\pi}{T}$ (rad/s)
RMS	$V_{rms} = \frac{V_m}{\sqrt{2}} = 0.707 V_m$ (sinusoids only)
Phase lead/lag	$\phi = \theta_v - \theta_i$. $\phi > 0$: v leads i (inductive). $\phi < 0$: i leads v (capacitive). $\Delta\phi = \omega\Delta t$.

PHASORS

Phasor	$\mathbf{V} = V\angle\theta$ — magnitude + phase at a fixed ω ; time is dropped.
MUST DO FIRST	Put every source in one reference form (all sine or all cosine) before reading off angles.
Identity	$\sin(\omega t + \theta) = \cos(\omega t + \theta - 90^\circ)$; $-\sin(x) = \sin(x \pm 180^\circ)$ — a minus sign is a 180° shift.
Magnitude	State whether you're using peak or RMS phasors and stay consistent ; AC power formulas below assume RMS.

COMPLEX ARITHMETIC

Engineering	$j = \sqrt{-1}$ (never i — that's current)
Rect $\rightarrow$ polar	$ Z = \sqrt{R^2 + X^2}$, $\angle Z = \arctan \frac{X}{R}$ (if $R < 0$, add 180° — calculators only return $\pm 90^\circ$)
Polar $\rightarrow$ rect	$Z = Z \cos \theta + j Z \sin \theta$
+/- vs $\times/\div$	+/- use rectangular . $\times/\div$ use polar : multiply/divide magnitudes, add/subtract angles.
j powers	$j^2 = -1$, $\frac{1}{j} = -j$, $j = 1\angle 90^\circ$

COMPLEX IMPEDANCE

Phasor Ohm	$\mathbf{V} = \mathbf{Z}\mathbf{I}$
Resistor	$Z_R = R = R\angle 0^\circ$ — v , i in phase
Inductor	$Z_L = j\omega L = \omega L\angle 90^\circ$ — v leads i by 90°
Capacitor	$Z_C = \frac{j}{\omega C} = \frac{1}{\omega C}\angle -90^\circ$ — i leads v by 90°
Reactance	$X_L = \omega L$, $X_C = -\frac{1}{\omega C}$; $Z = R + jX$; $Y = 1/Z = G + jB$ (S). $\omega \rightarrow 0$: $Z_L \rightarrow 0$, $ Z_C \rightarrow \infty$ (matches DC). $\omega \rightarrow \infty$: reverse.

AC CIRCUIT ANALYSIS

1	Fix ω ; convert every source to a phasor and every R/L/C to an impedance.
2	Every DC technique applies unchanged with Z for R : series/parallel, dividers, node, mesh, Thévenin, superposition.
3	Do the complex algebra (polar for $\times/\div$, rectangular for $+/ -$).
Z_{Th}	same rules as R_{Th} , complex-valued. Series RLC: $Z = R + j(\omega L - \frac{1}{\omega C})$.
Resonance	$\omega_0 = \frac{1}{\sqrt{LC}}$: X cancels, $Z = R$ (purely real, PF= 1). $ \mathbf{V}_L , \mathbf{V}_C $ can each exceed the source — normal, not an error.

AC POWER (RMS VALUES)

Real	$P = V_{rms} I_{rms} \cos \phi$ (W) — only R dissipates
Reactive	$Q = V_{rms} I_{rms} \sin \phi$ (VAR) — stored/returned by L and C
Apparent	$S = V_{rms} I_{rms} = \sqrt{P^2 + Q^2}$ (VA)
Δ Peak vs RMS	These need RMS. With peak phasors, $P = \frac{1}{2} V_m I_m \cos \phi$.
Power factor	PF = $\cos \phi = \frac{P}{S}$, $0 \leq \text{PF} \leq 1$. Lagging = inductive (i lags v); leading = capacitive (i leads v).

COMPLEX POWER & TRIANGLE

Complex power	$\mathbf{S} = \mathbf{V}_{rms} \mathbf{I}_{rms}^* = P + jQ = S\angle\phi$
Note	The conjugate on $\mathbf{I}$ is what makes $\angle \mathbf{S} = \theta_v - \theta_i$. Forgetting it flips the sign of Q .
Conservation	P and Q each add over all elements: $\sum P = 0$, $\sum Q = 0$. S does not add arithmetically.
Δ Q sign	With $\phi = \theta_v - \theta_i$ and $\mathbf{S} = \mathbf{V}_{rms} \mathbf{I}_{rms}^*$: $Q > 0$ for an inductive (lagging) load, $Q < 0$ for capacitive (leading) — matches the course's own worked example ($\mathbf{V} = 120\angle 30^\circ$, $\mathbf{I} = 10\angle 0^\circ$, lagging, $Q = +600$ VAR). One slide bullet states the opposite rule in words; trust this formula and the worked numbers over that bullet.
PF correction	Add C in parallel to cancel inductive Q ; P unchanged, S drops, PF $\rightarrow 1$.

IDEAL OP-AMP

R_{in}	$\infty \Rightarrow$ no current into either input
R_{out}	$0 \Rightarrow$ ideal voltage source at the output
Golden rules	With negative feedback : $v_+ = v_-$ (virtual short) and $i_+ = i_- = 0$.
Virtual ground	If $+$ is tied to ground, then $v_- = 0$ V — but it is <i>not</i> a real ground; no current sinks into it.
Saturation	Output clips at the supply rails $\pm V_{CC}$; the golden rules stop holding there.

INVERTING AMPLIFIER

Circuit	$+$ to ground; v_{in} through R_{in} to the $-$ node; R_f from output back to $-$.
Gain	$A_v = \frac{v_{out}}{v_{in}} = -\frac{R_f}{R_{in}}$
Minus sign	180° inversion — positive in, negative out. Do not drop it.
Example	$R_f = 10$ k Ω , $R_{in} = 1$ k $\Omega \Rightarrow A_v = -10$; 1 V in gives -10 V out. Always verify $ v_{out} \leq V_{CC}$, else it saturates.

EXAM GOTCHAS – FINAL CHECK

Signs	PSC: current into $\Rightarrow$ absorbing. Node KCL: all currents leaving. Mesh: all clockwise. Deactivating: V-src $\rightarrow$ short, I-src $\rightarrow$ open, dependent sources never.
Units & mode	Convert k Ω / μ F/mH <i>before</i> substituting (k Ω $\times$ mA=V; k Ω $\times$ μ F=ms). Check degrees-vs-radians before every phasor problem.
Continuity & RMS	v_C, i_L continuous at $t = 0$, everything else can jump. Power formulas want RMS, not peak. Superposition never for power directly.
Verify	KCL at one node + KVL around one loop + $\sum p = 0$ catches most arithmetic slips.